

Hardware Interfacing

230 V AC MAINS SUPPLY



AC Motor

----- ZMPT101B(Voltage sensor)

(L ,N of VS connected to Mains Supply L,N)

----- WCS1700(Current sensor)



(live wire passing through the hall sensor)

----- DHT 22(Temperature sensor)

----- SW420(Vibration sensor)

(glued to the motor casing)


VIBRATION
SENSOR

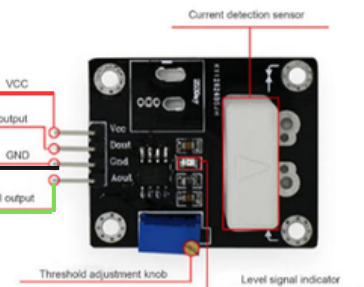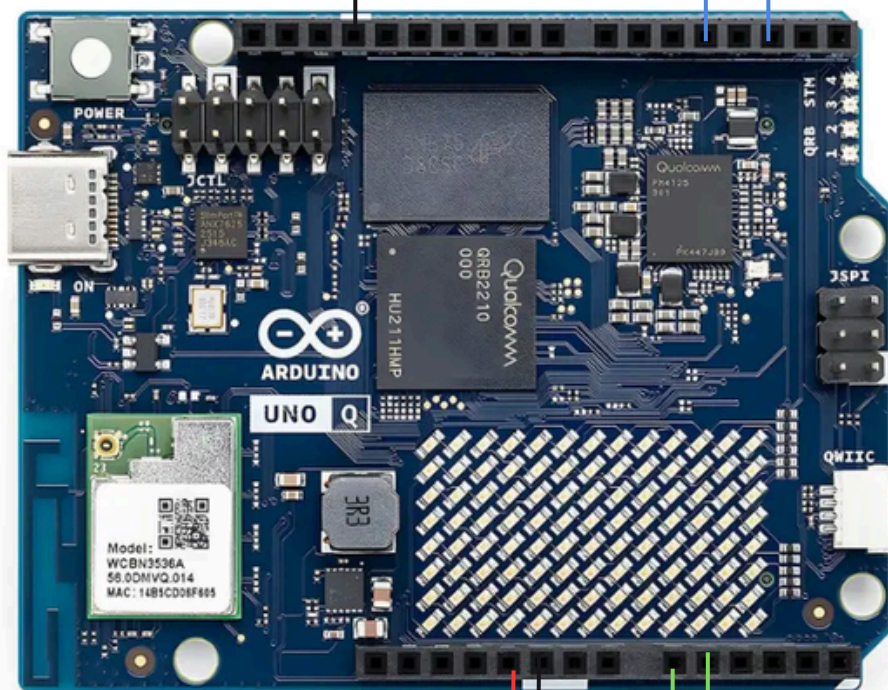

CURRENT
SENSOR




TEMPERATURE
SENSOR

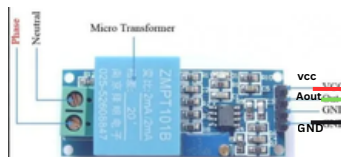


VOLTAGE
SENSOR

Hardware Configuration and Component Details


5V Supply

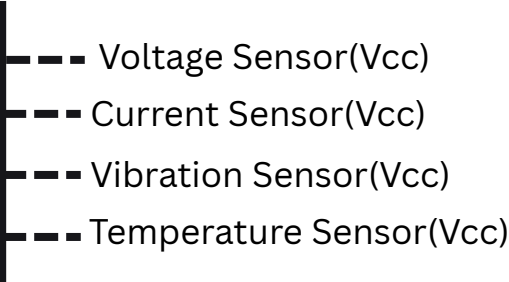


Common GND

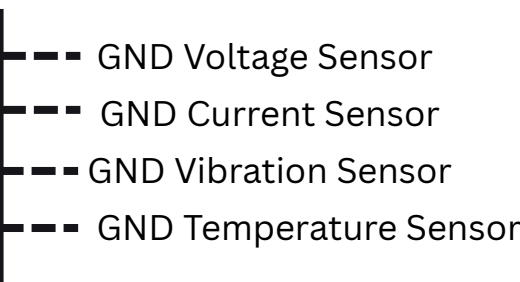

Digital Pins

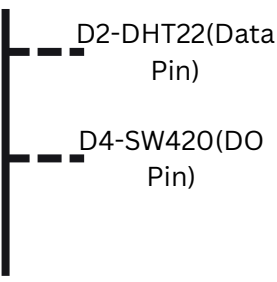

Analog Pins

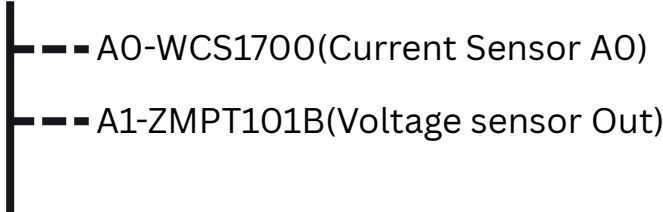

Component	Qty	Purpose
Arduino UNO Q	1	Controller
AC Motor	1	Test Machine
WCS1700	1	Current
ZMPT101B	1	Voltage
DHT22	1	Temperature
SW420	1	Vibration